

A_2_answer

April 14, 2020

Bioinstrumentation ENGG 6150 Assignment

Student: Jian Bin(Kevin), Lin

Instructor: Dr.Maher Bakri-Kassem

Q1:

$$R_a = R_d = R_o - Z * R_o = R_o(1 - Z)$$

$$R_o = \frac{R_a}{1-Z}$$

$$R_b = R_c = R_o = \frac{R_a}{1-Z} = \frac{R_d}{1-Z}$$

Output voltage has positive and negative output.

$$\frac{v_{O+}}{V_{ps}} = \frac{R_a}{R_a + R_b}$$

This is because positive voltage connects to R_b and R_a

Arrange formula

$$V_{O+} = \frac{V_{ps} R_o (1-Z)}{R_o (1-Z) + R_o}$$

R_o cancelled out from denominator and numerator

$$V_{O+} = \frac{V_{ps} (1-Z)}{(1-Z)+1}$$

$$V_{O+} = \frac{V_{ps} (1-Z)}{2-Z}$$

same principle apply to negative voltage side as it connects to R_c and R_d

$$\frac{v_{O-}}{V_{ps}} = \frac{R_d}{R_c + R_d}$$

Arrange formula

$$V_{O-} = \frac{V_{ps} R_o (1-Z)}{R_o (1-Z) + R_o}$$

R_o cancelled out from denominator and numerator

$$V_{O-} = \frac{V_{ps} (1-Z)}{(1-Z)+1}$$

$$V_{O-} = \frac{V_{ps} (1-Z)}{2-Z}$$

$$V_o = V_{O+} + V_{O-}$$

since negative node is “-”, therefore

$$V_o = \frac{V_{ps} (1-Z)}{2-Z} - \frac{V_{ps} (1-Z)}{2-Z} = 0$$

Output voltage does not depend on Z .

Alternatively, we can swap R_a with R_b or R_c with R_d .

Assume swap R_a with R_b Then

$$\frac{v_{O+}}{V_{ps}} = \frac{R_b}{R_a + R_b}$$

Arrange formula

$$V_{O+} = \frac{V_{ps} R_o}{R_o (1-Z) + R_o}$$

R_o cancelled out from denominator and numerator

$$V_{O+} = \frac{V_{ps} (1)}{(1-Z)+1}$$

$$V_{O+} = \frac{V_{ps} (1)}{2-Z}$$

$$\frac{v_{O-}}{V_{ps}} = \frac{R_d}{R_c + R_d}$$

Arrange formula

$$V_{O-} = \frac{V_{ps} R_o (1-Z)}{R_o (1-Z) + R_o}$$

R_o cancelled out from denominator and numerator

$$V_{O-} = \frac{V_{ps} (1-Z)}{(1-Z)+1}$$

$$V_{O-} = \frac{V_{ps} (1-Z)}{2-Z}$$

$$V_o = \frac{V_{ps} (1)}{2-Z} - \frac{V_{ps} (1-Z)}{2-Z}$$

Now output voltage depends on parameter Z .

```

In [36]: import numpy as np
import math
import matplotlib.pyplot as plt
#Assume outage, temperature are certain values, question tells us that
#temperature is inversely proportional to time and resistive is inversely
#propotional to temperature

V_out = range(2,20,2)

Time = range(1,10)

Temperature = range(10,1,-1)

Resistance = range(12,3,-1)

plt.plot(Time,V_out,label='output voltage vs time')
plt.xlabel('Time')
plt.ylabel('y-axixs')
plt.title('resistive temperature sensor')


plt.plot(Time,Temperature,label='Temperature vs time')

plt.plot(Time,Resistance,label='Sensor resistance vs temperature')

plt.legend()

```

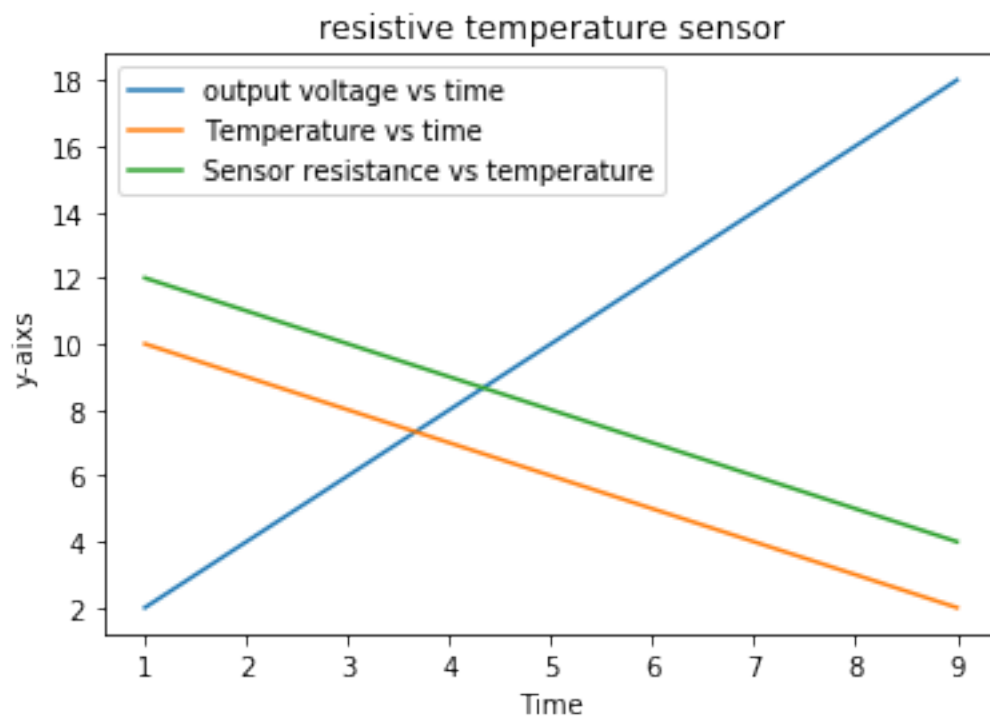Out[36]: <matplotlib.legend.Legend at 0x11422bc88>



In []: Q3:

ECG: Refers to ElectroCardioGram which **is** used to measure heart electronic potential. Place electrode on the surface of human body. When muscle contracts, it creates action potential, ECG machine shows potential difference.

EEG: Refers to ElectroEncephaloGram which **is** used to electrical activity **in** brain. Electrical discs are attached to brain. When brain cells communicate **with** each other, it generates electrical potential which can be scanned using EEG.

EMG: Refers to ElectroMyoGraphy which **is** used to measure muscle electron response based on muscle nerve cell response. When muscle **is** at rest, there **is** no potential activity going on. These nerve cells are called motor neurons. They transfer electrical signals **and** ask muscle to relax **or** contract.

ENG: Refers to ElectroNystagmoGraphy which **is** used to detect false sense of spinning **or** motion. Electrode has placed under **or** above the eye. The activity of eye motion has been recording **in** the machine. The electrical activity that controls eye movement have been recorded.

ERG: Refers to ElectroRetinoGraphy which **is** used to detect the function of retina. During the test, eye was forced to look at certain objects. Retina transmits the electrical signal which can be captured by the machine **and** generate voltage.